

# **Operational Amplifiers**

A brief introduction

## Op-Amp Introduction

- Need exists for a circuit element that can perform:
  - Add, subtract, multiply, divide, differentiate, integrate
- Evolved from Analog Computers
- Op-Amp properties
  - Single building block which can be assembled into above functions by adding passive components (R,L,C)
  - Inexpensive (used in high volume)
  - Compact
- Op-Amp analysis
  - Use assumptions of “Ideal Op-Amp” to allow low frequency performance to be approximated
  - Typically have near ideal characteristics but frequency response of an integrator ( $G(s) = 1/\tau s$ ). (Otherwise, the high bandwidth would be impossibly difficult to manage.)

# Ideal Op-Amp Assumptions

- Differential function


- $V_{out} = A \cdot \Delta V$

- Infinite

- Intrinsic gain:  $A = \infty$
  - Input impedance:  $Z_{in} = \infty$
  - Bandwidth:  $V_{out} \neq f(\omega)$

- Zero

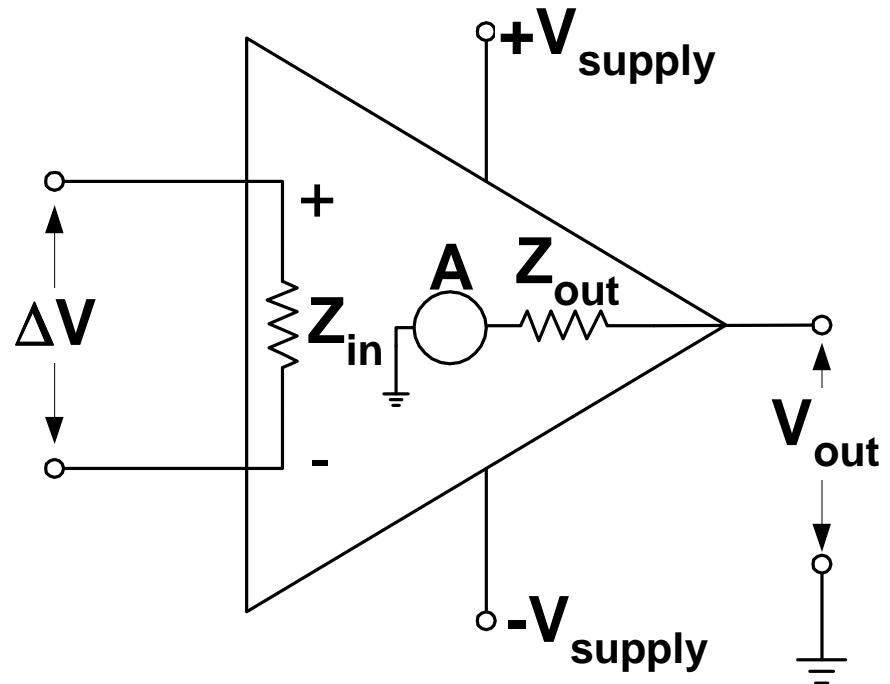- Input offset voltage:  $V_{io} = 0$  for  $V_{out} + V_{io} = A \cdot \Delta V$
  - Input impedance:  $Z_{out} = 0$




# Inverting Amplifier

- Consider the circuit configuration to the right

$$V_{in} = V_{R_{in}} + \Delta V + V_{R_b}$$

$$V_{out} = V_{R_f} + \Delta V + V_{R_b}$$
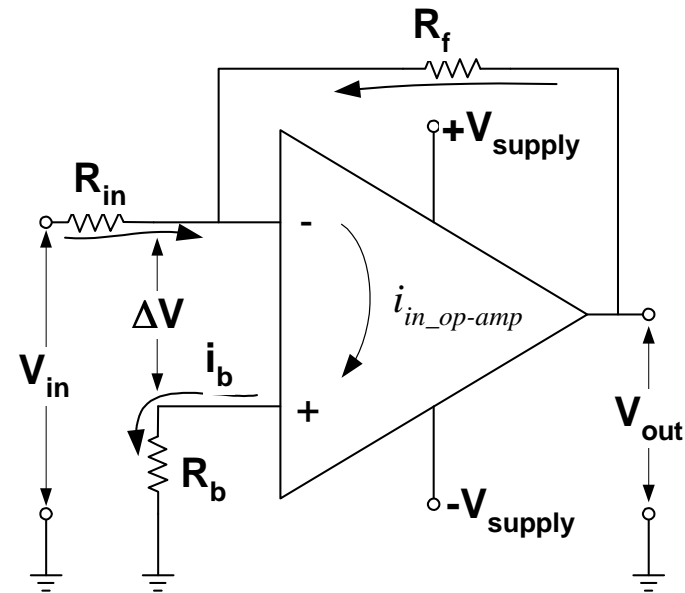
$$i_{R_{in}} + i_{R_f} = i_{in\_op-amp}$$



- Assuming intrinsic gain of the op-amp is very large for the frequency of interest:  $\Delta V A = V_{out}$ 
  - $V_{out}$  is finite and typically within +15 to -15 V implying  $\Delta V$  is very small
- Assuming  $i_b$  is very small given the intrinsic input impedance is very large,  $V_b$  must be very small

## Inverting Amplifier

$$\begin{aligned} V_{in} &\cong V_{R_{in}} & \frac{V_{R_{in}}}{R_{in}} &= -\frac{V_{R_f}}{R_f} \\ V_{out} &\cong V_{R_f} & \frac{V_{in}}{R_{in}} &= -\frac{V_{out}}{R_f} \end{aligned} \quad \boxed{\frac{V_{out}}{V_{in}} = -\frac{R_f}{R_{in}}}$$

- Amplifier performance is a function of external components only for ideal assumptions
- Input and output impedances of the amplifier can be calculated as approximately:

$$Z_{in} = R_{in} \quad Z_{out} = \frac{Z_{out\_intrinsic}}{\left(1 + A \frac{R_{in}}{R_{in} + R_f}\right)}$$

- Very good output impedance characteristics

## Non-Inverting Amplifier

$$V_{in} = V_{R_{in}} + \Delta V + V_{R_b}$$

$$V_{out} = V_{R_f} + V_{R_b}$$


$$i_{R_f} + i_b = i_{R_b}$$

$$V_{in} \cong V_{R_b}$$

$$V_{out} = V_{R_f} + V_{in}$$

$$i_{R_f} \cong i_{R_b} \quad \frac{V_{R_f}}{R_f} = \frac{V_{R_b}}{R_b} \quad V_{R_f} = V_{in} \frac{R_f}{R_b}$$
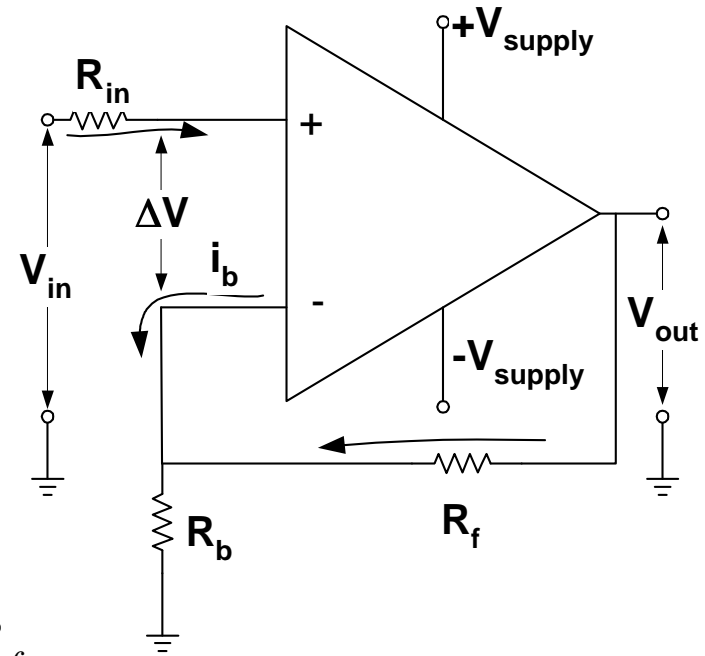
$$V_{out} = V_{in} \frac{R_f}{R_b} + V_{in} = V_{in} \left( 1 + \frac{R_f}{R_b} \right)$$



$$\frac{V_{out}}{V_{in}} = \left( 1 + \frac{R_f}{R_b} \right)$$

## Non-Inverting Amplifier

- Input and output impedances can be calculated as approximately:

$$Z_{in} = Z_{in\_intrinsic} \left( 1 + A \left( \frac{R_{in}}{R_{in} + R_f} \right) \right)$$

$$Z_{out} = \frac{Z_{out\_intrinsic}}{\left( 1 + A \left( \frac{R_{in}}{R_{in} + R_f} \right) \right)}$$

# Differentiator

- Consider the circuit configuration to the right

$$V_{in} = V_{C_{in}} + \cancel{\Delta V} + \cancel{V_{R_b}}$$

$$V_{out} = V_{R_f} + \cancel{\Delta V} + \cancel{V_{R_b}}$$

$$i_{C_{in}} + i_{R_f} = \cancel{i_{in\_op-amp}}$$


$$i_{C_{in}} = C_{in} \frac{dV_{C_{in}}}{dt}$$

$$i_{C_{in}} = C_{in} \frac{dV_{C_{in}}}{dt} = -i_{R_f} = \frac{V_{R_f}}{R_f}$$

$$i_{R_f} = \frac{V_{R_f}}{R_f}$$


$$C_{in} \frac{dV_{in}}{dt} = \frac{V_{out}}{R_f}$$
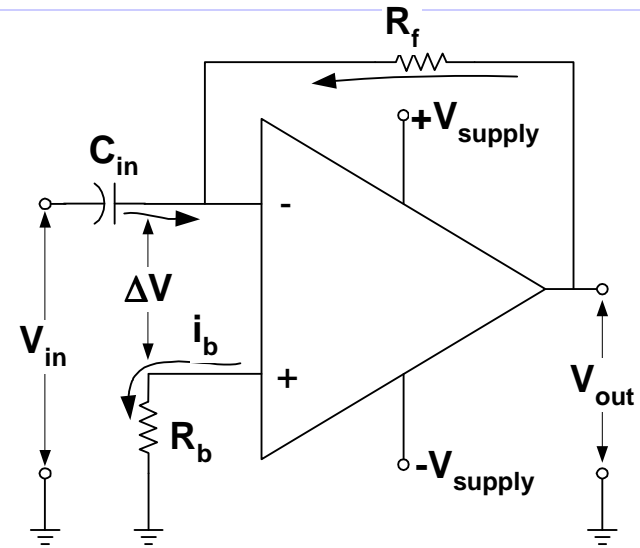
$$V_{out} = R_f C_{in} \frac{dV_{in}}{dt}$$


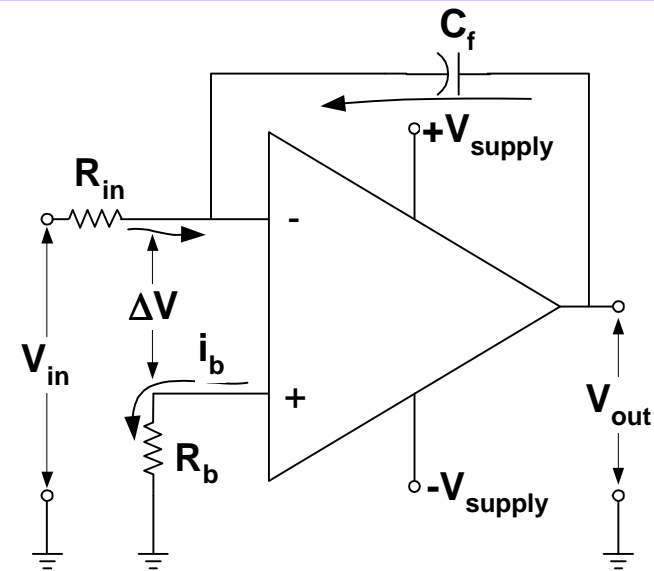
# Integrator

- Consider the circuit configuration to the right



$$V_{in} = V_{R_{in}} + \Delta V + V_{R_b}$$

$$V_{out} = V_{C_f} + \Delta V + V_{R_b}$$

$$i_{R_{in}} + i_{C_f} = i_{in\_op-amp}$$

$$i_{C_f} = C_f \frac{dV_{C_f}}{dt}$$

$$i_{R_{in}} = \frac{V_{R_{in}}}{R_{in}}$$

$$i_{R_{in}} = \frac{V_{R_{in}}}{R_{in}} = -i_{C_f} = C_f \frac{dV_{C_f}}{dt}$$

$$\frac{V_{in}}{R_{in}} = C_f \frac{dV_{out}}{dt}$$

$$\int V_{in} dt = R_{in} C_f \int dV_{out}$$

$$V_{out} = \frac{1}{R_{in} C_f} \int V_{in} dt$$

# What is the transfer function for this circuit?

